

Today's Discussion

How do we add support for new instructions (aka processor extensions) to a processor?

2 things to consider:

- Datapath
- Control Logic

Review: What is available in our datapaths?

- Program Counter (PC)
- Memory
 - Separate Instruction and Data memory for Single Cycle
 - Combined (Von Neumann) Instruction + Data memory for Multi Cycle
 - Data memory has read and write capability
- Register File
 - Read and write capability
- Arithmetic and Logic Unit (ALU), extra adders for single cycle
- Muxes, wires, control Logic
- For the Multi Cycle: registers to hold intermediate values

EECS 370

Fall 2024

3

EECS 370

Fall 2024

4

Tricks with the ALU

Remember these tricks from Lab 2:

$\text{NOR}(X, X) == \text{NOR}(X, 0) == \sim X$
 $\sim(\text{NOR}(X, Y)) == \sim(\sim(X \mid Y)) == X \mid Y$
 $\text{NOR}(\sim X, \sim Y) == \sim(\sim X \mid \sim Y) == X \& Y$
 $X + (\sim Y + 1) == X + (\sim Y) == X - Y$
 $X + X == X * 2 == X \ll 1$
 $X * 2^Y == X \ll Y$

EECS 370

Fall 2024

5

Components used by each Opcode

cheat sheet

Instr.	Read PC, Access Instr. Mem.	Read Reg.	ALU	Data Mem. Access	Write PC	Write Reg.
add	✓	✓	✓			✓
nor	✓	✓	✓			✓
lw	✓	✓	✓	✓ (Read)		✓
sw	✓	✓	✓	✓ (Write)		
beq	✓	✓	✓x2		✓	
jair	✓	✓			✓	✓
noop	✓					
halt	✓					

EECS 370

Fall 2024

6

EECS 370

Fall 2024

7

Review: Single vs Multi Cycle

For Single Cycle:


- Simplified logic since there is 1 cycle per instruction
- If we need a component twice, we must **duplicate** it

For Multi Cycle:

- 2+ cycles per instruction, must define **control logic** per cycle
- If we need a component twice, use it in different cycles
- Attempt to parallelize independent tasks on different components

For both: only 1 value can be on a wire in any cycle. Every wire should only have 1 input. Adding a mux allows multiple inputs

LC2K Single-Cycle Datapath

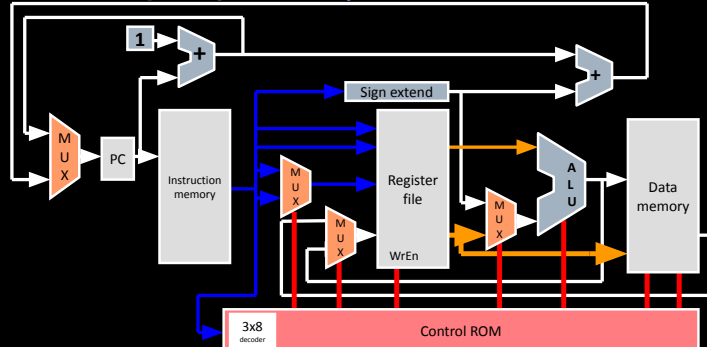

EECS 370

Fall 2024


8

EECS 370

Fall 2024


9

LC2K Multi-cycle Datapath

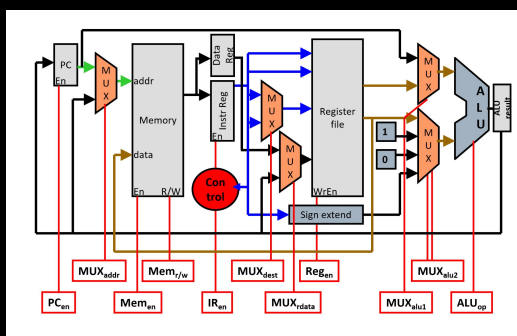

Multi-Cycle State Machine

- Noop goes back to fetch (state 0) after decode (state 1)
- Halt stops in decode (state 1)

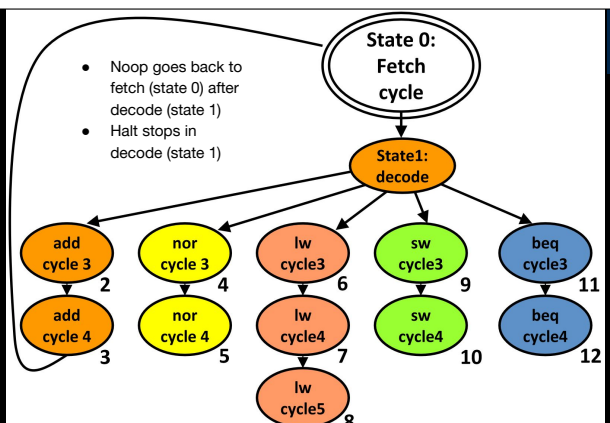

EECS 370

Fall 2024


9

EECS 370


Fall 2024

10

8-entry 4-bit ROM

 

Use a ROM to Select Inputs in Our MUXes

 

The ROM specifies which inputs and outputs each component uses for each state

Performance

IRON LAW: Execution Time = #Instructions * CPI * ClockPeriod = #Cycles * ClockPeriod

Clock Period

- Single Cycle: Latency of Slowest Instruction
- Multi Cycle: Latency of Slowest Cycle (generally slowest datapath component)

#Cycles

- Single Cycle: #Instructions
- Multi Cycle: #Instructions * sum over all opcodes(%opcodes*cycles for opcode)

CPI

- Single Cycle: 1 (it's in the name)
- Multi Cycle: #Cycles/#Instructions

#Cycles Per Opcode (MULTICYCLE ONLY)

- add/nor/sw/beq: 4 cycles
- lw: 5 cycles
- noop/halt: 2 cycles
- jalr: Don't worry about it

Lab Assignment Problem 2

We need to add this instruction to the single cycle datapath:

$[destReg] = memory[2 * [regB]]$

Each operator in the C expression will tell us which components and inputs we need.

For example, we can convert: $2 * [regB] \rightarrow [regB] + [regB]$

Our datapath allows us to add, but we can't add regB to regB!

Need to modify the inputs to fix.

Lab Assignment Problem 2

After modifying the datapath, we can order the steps to execute the instruction:

$[destReg] = memory[[regB] + [regB]]$

- Fetch Instruction from Memory (ALWAYS!)
- Read registers, i.e. regB
- Add regB to regB (output wire is ALU result)
- Load memory at ALU result
- Write memory result to register, i.e. destReg

Then, you can write the control ROM for these steps.

Lab Assignment Problem 3


We need to add this instruction to the multi cycle datapath:

$[regB] = -memory[[regA] + offset]$

What's here or missing?

- We can fetch and read registers
- We can add regA to offset
- We can load memory at the ALU result
- We can write to regB from the ALU or memory
- Missing: we need to do ALU ops on memory and intermediate results from the ALU. $-mem == \sim(mem \mid 0) + 1$

Problem 3 Multi Cycle FSM

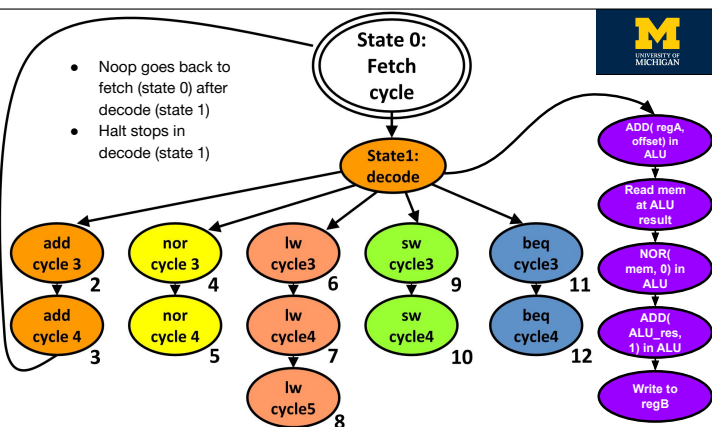

On the exam, you will be expected to:

- Parse the instruction
- Define steps & cycles
- Modify the datapath
- Write the control ROM